

Cambridge Technicals Engineering

Unit 4: Principles of electrical and electronic engineering

Level 3 Cambridge Technical Certificate/Diploma in Engineering
05822 - 05825

Mark Scheme for January 2020

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.

© OCR 2020

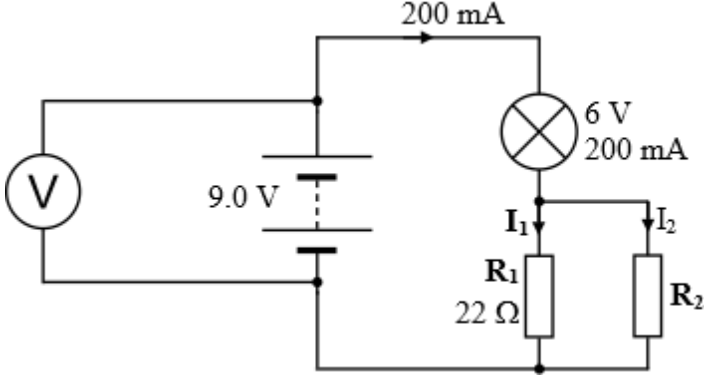

Annotations


<i>Annotation</i>	<i>Meaning</i>
tick	Correct response
cross	Incorrect response
Omission mark (carat)	Incomplete response
ECF	Error carried forward
BOD	Benefit of doubt
NBOD	No benefit of doubt
RE	Rounding error

Subject-specific marking instructions

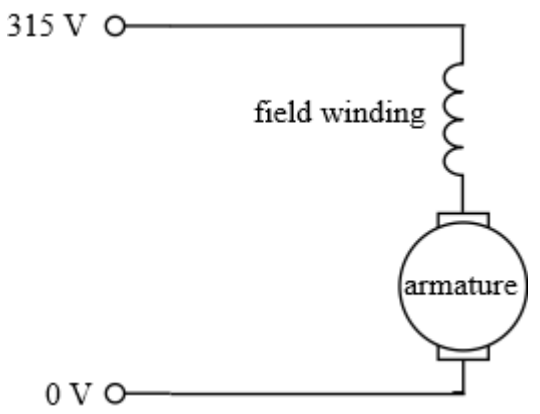
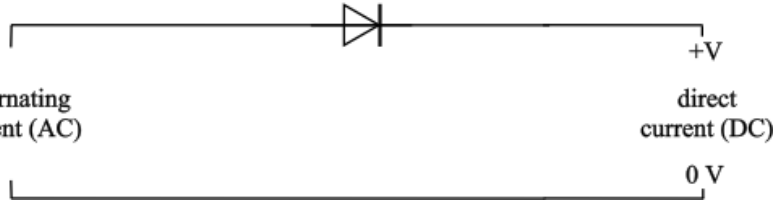







- In all numerical calculation questions a correct response will gain all marks unless specified otherwise.
- Rounding of answers should be to the same number of significant figures as the data in the question, or, otherwise, an answer will be correct provided it rounds to the correct answer.
- Symbols used in circuit diagrams must identify relevant components uniquely and unambiguously.

Question		Answer	Marks	Guidance
1	(a)	$P = VI = 6 \times 0.2 = 1.2 \text{ (W)}$	1	
1	(b)	$3 \text{ minutes} = 180 \text{ s}$ $E = P \Delta t$ (Evidence of using correct equation) $= 1.2 \times 180 = 216$ (Correct calculation) J or Joules (Correct units)	1 1 1	Ecf for P from 1(a) Synoptic mark from Unit 2: 3.8 Accept alternative calculation consistent with units. Accept valid units of energy (J, Ws, Wmin, Whr) provided consistent with calculation. Synoptic mark from Unit 2:1.1
1	(c)	$9 - 6 = 3 \text{ (V)}$	1	
1	(d)	$I_1 = \frac{3}{22} = 0.136 \text{ A} = 136 \text{ (mA)} = 140 \text{ (mA)} \text{ (2 s.f.)}$	1	Ecf for their 1 (c)
1	(e)	$I_2 = 200 - I_1 = 0.064 \text{ A}$ $R_2 = \frac{V \text{ across } R_2}{I_2} = 47 \text{ (}\Omega\text{)}$	1 1	Evidence of calculating I_2 ie award use of Kirchoff I (ecf for their I_1) Correct calculation using Ohm's law and their 1(c) ecf I_2
1	(f)	$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{22} + \frac{1}{47} = 0.0667$ $\frac{1}{0.0667} = 15 \text{ (}\Omega\text{)} \pm 1 \Omega \text{ (i.e. } 14 \Omega \text{ to } 16 \Omega\text{)}$	1	Ecf for their R_2 from 1 (e)


Question			Answer	Marks	Guidance
1	(g)		Voltmeter connected across battery	1	
2	(a)	(i)		<p>1</p> <p>1</p> <p>1</p>	<p>Indication of AC power supply with value shown</p> <p>3 components in series and correct symbol for resistor with value shown</p> <p>Correct symbol for capacitor with value shown</p> <p>Symbols clear enough that they couldn't be mistaken for another component eg length of capacitor lines</p>
2	(a)	(ii)	<p>$f = 250 \text{ kHz} = 250000 \text{ Hz}$</p> <p>$C = 220 \text{ pF} = 2.2 \times 10^{-10} \text{ F}$</p> $\frac{1}{2\pi fC} = \frac{1}{2\pi \times 250000 \times 2.2 \times 10^{-10}} = 2900 \text{ } (\Omega)$	<p>1</p> <p>1</p> <p>1</p>	<p>Correct conversion to Hz</p> <p>Correct conversion to F</p> <p>(ecf from value for f and C)</p>

Question			Answer	Marks	Guidance
2	(a)	(iii)	$Z = \sqrt{R^2 + X_C^2} = \sqrt{4700^2 + 2900^2}$ <p>Correct values in equation.</p> <p>$Z = 5519 = 5500 \text{ } (\Omega) \text{ (2 s.f.)}$</p>	1 1	Allow ecf from 2a(ii)
2	(a)	(iv)	$(\cos \phi) = \frac{4700}{5519} = 0.852$ <p>$\cos^{-1}(0.852) = 31.6^\circ \pm 1$</p>	1 1	Allow ecf from 2a(iii) Correct calculation of arc cos Synoptic mark from unit 1:4.7
3	(a)		<p>Diagram with labelled field winding, labelled armature and no other parts (with exception of a load resistor) and current supplied to armature.</p> <p>Field winding and armature in series with power supply.</p>	1 1	 <p>315 V ○ ———— field winding ———— armature ———— 0 V ○</p> <p>Accept any unambiguous labelled symbols</p>

Question			Answer	Marks	Guidance
3	(b)		Valid comment about torque or turning force Valid comment about conditions e.g. starting from rest/low speed E.g. Series wound motor develops high torque (wtte) At low speed (wtte) Or Shunt wound motor has low torque (wtte) On starting (wtte)	1 1	
3	(c)	(i)	Resistance of motor = $R_a + R_f = 0.42 + 0.63 = 1.05 \text{ } (\Omega)$	1	
3	(c)	(ii)	$I_a = \frac{V-E}{R_a+R_f}$ $I_a = \frac{315-141}{1.05} = 165.71 = 166 \text{ (A) (3 s.f.)}$	1 1	evidence of correctly rearranging formula Synoptic mark from unit 1: 1.3 correct substituting and calculating. ecf for their 3ci
3	(c)	(iii)	Current increases Up to 2 marks for explanation: EMF decreases Link to motor equation i.e. I increases as E decreases due to R/V staying the same	1 1 1	Must be correct to be awarded explanation marks.

Question	Answer	Marks	Guidance
<p>4 (a) (i)</p>	<p>Correct diode symbol  used anywhere in diagram</p> <p>Diodes achieve rectification</p> <p>Connections are made so that rectifier produces correct polarity half-wave rectified dc</p> <p>Correct answers for 3 marks:</p> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;">  </div> <div style="text-align: center;">  </div> </div>	<p>1</p> <p>1</p> <p>1</p>	<p>Accept alternative diode symbol</p> <div style="display: flex; justify-content: space-around;">    </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;">    </div> <p>Award this mark even if polarity of output is incorrect</p> <p>Must obtain rectification mark for this mark</p>

Question			Answer	Marks	Guidance								
4	(a)	(ii)	Comment about diode only conducting in one direction	1	Diode only conducts/allows current to flow/allows appropriate wave cycle through (or wtte) in one direction So only allows positive part of AC signal (allow description of current flow that makes it clear correct polarity is achieved) through to the output (or wtte)								
			Comment about only half of ac wave being conducted to output	1									
4	(b)		Maintains constant/little change in voltage/current (wtte)	1	Do not allow power								
			Regardless of the load on the output (wtte)	1	Accept 'regardless of current drawn' if constant or little change in voltage								
4	(c)		Fuses are used to protect power supplies and electrical devices. A fuse is connected in series with the power supply and the electrical device. If a fault occurs in the electrical device and it draws too much power then high current flows through the fuse causing it to get very hot and melt. After the fuse has melted no current is supplied to the electrical device and it stops operating.	1 1 1									
5	(a)		One mark for each correct answer	4	Allow symbol for infinite								
			<table border="1"> <thead> <tr> <th>Ideal op-amp</th> <th>Real op-amp</th> </tr> </thead> <tbody> <tr> <td>infinite (1)</td> <td>very high</td> </tr> <tr> <td>infinite (1)</td> <td>high (1)</td> </tr> <tr> <td>zero</td> <td>low (1)</td> </tr> </tbody> </table>			Ideal op-amp	Real op-amp	infinite (1)	very high	infinite (1)	high (1)	zero	low (1)
			Ideal op-amp			Real op-amp							
			infinite (1)			very high							
			infinite (1)			high (1)							
zero	low (1)												

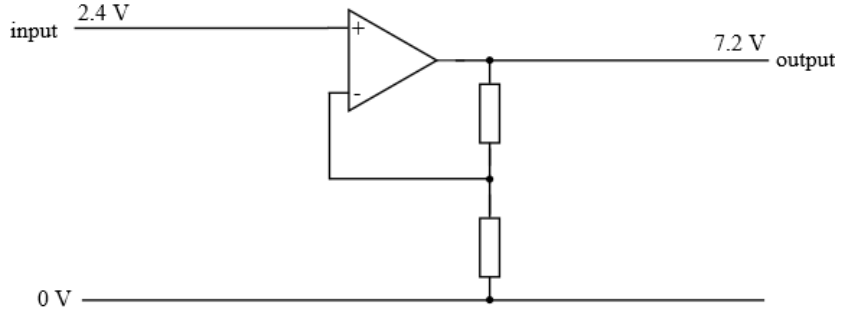Question			Answer	Marks	Guidance
5	(b)	(i)	 <p>input 2.4 V</p> <p>7.2 V output</p> <p>0 V</p>	1	Allow arrow from 0V up to positive rail
5	(b)	(ii)	non-inverting amplifier	1	
5	(b)	(iii)	$Voltage\ Gain = \frac{7.2}{2.4} = 3.0$	1	Synoptic mark from unit 1: 1.3 Ignore units
5	(b)	(iv)	Resistors in ratio 2:1 Larger value labelled on top resistor Units in Ω [or $k\Omega$]	1 1 1	Synoptic mark from unit 2: 1.1

Question		Answer	Marks	Guidance
6	(a)	<p>1 mark for each correct line</p> <p style="text-align: center;">Start of sentence end of sentence</p> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <p>A rising-edge D type flip-flop is triggered when the clock <u>changes</u>..</p> <p>When a D type bi-stable flip-flop is triggered the information is <u>copied</u>..</p> </div> <div style="width: 45%; text-align: right;"> <p>.. from D to Q</p> <p>.. from 0 to 1</p> <p>.. from 1 to 0</p> <p>.. from Q to D</p> </div> </div>	2	
6	(b)		1	Gate and labels are needed for the mark

Question		Answer	Marks	Guidance															
6	(c)	<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table> <p>All combinations of A and B (any order) Q correct</p>	A	B	Q	0	0	0	0	1	1	1	0	1	1	1	0	1 1	
A	B	Q																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
6	(d)	$Q = A \oplus B$	1																

Question		Answer	Marks	Guidance																																				
6	(e)	<table border="1"> <thead> <tr> <th>G</th> <th>H</th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	G	H	J	K	1	1	1	1	1	1	1	1	1	0	1	1	1	0	0	0	0	0	1	1	0	0	1	1	0	1	1	1	0	1	0	1	<p>1</p> <p>1</p> <p>1</p> <p>1</p>	<p>1 mark for each correct column</p> <p>G</p> <p>H - allow ecf from G to H (if 0 scored for G)</p> <p>J</p> <p>K - allow ecf from H and J to K (if 0 scored for J)</p>
G	H	J	K																																					
1	1	1	1																																					
1	1	1	1																																					
1	0	1	1																																					
1	0	0	0																																					
0	0	1	1																																					
0	0	1	1																																					
0	1	1	1																																					
0	1	0	1																																					

OCR (Oxford Cambridge and RSA Examinations)
The Triangle Building
Shaftesbury Road
Cambridge
CB2 8EA

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2020

