

Cambridge Technicals Engineering

Unit 4: Principles of electrical and electronic engineering

Level 3 Cambridge Technical Certificate/Diploma in Engineering
05822 - 05825

Mark Scheme for January 2022

OCR (Oxford Cambridge and RSA) is a leading UK awarding body, providing a wide range of qualifications to meet the needs of candidates of all ages and abilities. OCR qualifications include AS/A Levels, Diplomas, GCSEs, Cambridge Nationals, Cambridge Technicals, Functional Skills, Key Skills, Entry Level qualifications, NVQs and vocational qualifications in areas such as IT, business, languages, teaching/training, administration and secretarial skills.

It is also responsible for developing new specifications to meet national requirements and the needs of students and teachers. OCR is a not-for-profit organisation; any surplus made is invested back into the establishment to help towards the development of qualifications and support, which keep pace with the changing needs of today's society.

This mark scheme is published as an aid to teachers and students, to indicate the requirements of the examination. It shows the basis on which marks were awarded by examiners. It does not indicate the details of the discussions which took place at an examiners' meeting before marking commenced.

All examiners are instructed that alternative correct answers and unexpected approaches in candidates' scripts must be given marks that fairly reflect the relevant knowledge and skills demonstrated.

Mark schemes should be read in conjunction with the published question papers and the report on the examination.



© OCR 2022


Annotations

<i>Annotation</i>	<i>Meaning</i>
tick	Correct response
cross	Incorrect response
Omission mark (carat)	Incomplete response
ECF	Error carried forward
BOD	Benefit of doubt
NBOD	No benefit of doubt
RE	Rounding error

Subject-specific marking instructions

- In all numerical calculation questions a correct response will gain all marks unless specified otherwise.
- Rounding of answers should be to the same number of significant figures as the data in the question, or, otherwise, an answer will be correct provided it rounds to the correct answer.
- Symbols used in circuit diagrams must identify relevant components uniquely and unambiguously.

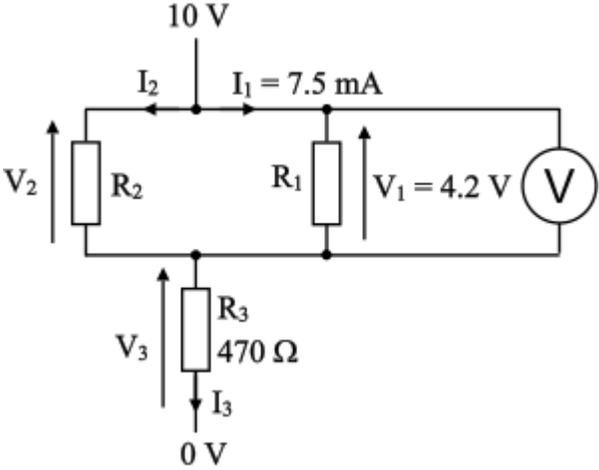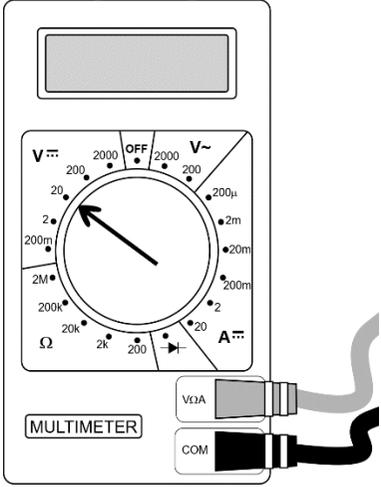Question	Answer	Marks	Guidance
<p>1 (a) (i)</p>	<p>Voltmeter symbol connected across R_1</p> 	<p>1</p>	<p>Any unambiguous symbol for voltmeter</p>
<p>1 (a) (ii)</p>	<p>Arrow pointing to 20 V ∴</p> 	<p>1</p>	
<p>1 (b)</p>	<p>$R_1 = 4.2/0.0075 = 560 \Omega$</p>	<p>1</p>	

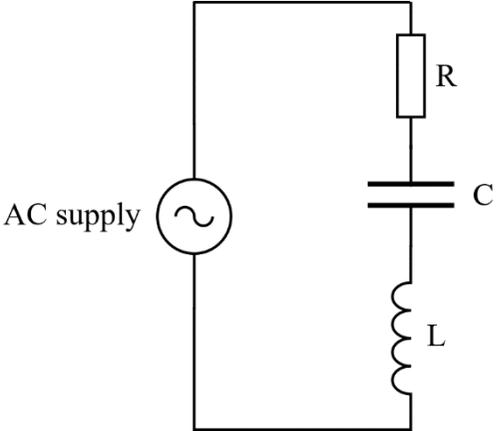Question			Answer	Marks	Guidance
2	(a)	(i)	<p>Four components in series correctly labelled</p> <p>Correct symbol for resistor, capacitor and inductor</p>  <p>The diagram shows a rectangular circuit loop. On the left vertical wire is a circle containing a tilde symbol (~), labeled 'AC supply'. On the top horizontal wire is a rectangle labeled 'R'. On the right vertical wire, from top to bottom, are two parallel horizontal lines labeled 'C' and a coil labeled 'L'. The bottom horizontal wire is a simple line.</p>	<p>1</p> <p>1</p>	<p>Accept AC or supply for the AC supply but not frequency alone. Order of components unimportant</p>
2	(a)	(ii)	<p>$f = 455 \text{ kHz} = 455000 \text{ Hz}$ Correct conversion to Hz</p> <p>$L = 240 \text{ } \mu\text{H} = 2.4 \times 10^{-4} \text{ H}$ Correct conversion to H</p> <p>$X_L = 2\pi fL = 2\pi \times 455000 \times 2.4 \times 10^{-4} = 686 \text{ } \Omega$</p>	<p>1</p> <p>1</p> <p>1</p>	<p>Synoptic mark from Unit 2: 1.1 (only penalise incorrect conversion of kHz to Hz once in question 2)</p> <p>Correct numerical answer (ecf for f and L)</p>


Question			Answer	Marks	Guidance
2	(a)	(iii)	$C = \frac{1}{2\pi \times 455000 \times 910} = 3.84 \times 10^{-10}$ $C = \frac{1}{2\pi f X_C}$ $C = 3.84 \times 10^{-10} \text{ F}$	1 1 1	<p>Correct substitution (only penalise incorrect conversion of kHz to Hz once in question 2 ie ecf for frequency)</p> <p>Evidence of correctly rearranging the formula Synoptic mark from Unit 1: 1.3</p> <p>Correct answer (with ecf) with consistent unit Synoptic mark from Unit 2: 3.15 Accept alternative units $C = 384 \text{ pF}$ $= 0.384 \text{ nF}$ $= 0.000384 \text{ } \mu\text{F}$ $= 0.000000000384 \text{ F}$</p> <p>Max 2 marks if incorrect or no unit given.</p>
		(iv)	$Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{330^2 + (910 - 686)^2}$ <p>Correct values in correct equation</p> $Z = 398.8 \text{ } \Omega$	1 1	<p>Allow ecf from 2(a)(ii) for their X_L (only penalise incorrect conversion of kHz to Hz once in question 2)</p>
		(v)	$I = V/Z = 15 / 398.8 = 0.0376\text{A}$	1	<p>Allow ecf from 2(a)(iv) for their Z</p>

Question		Answer	Marks	Guidance
3	(a)		1 1	Both circuit symbols drawn correctly Field winding and armature in parallel with power supply. Ignore any additional resistor symbols.
3	(b)	<p>reduced increased constant</p>	1 1 1	A shunt-wound DC motor maintains a fairly constant speed regardless of load. When the motor is running with no load it spins at high speed. When a load is applied to the motor the speed reduces and the EMF generated in the armature is <i>reduced</i> , this means that the current in the armature is increased and so the torque is <i>increased</i> . The current in the field winding is <i>constant</i> . All of this keeps the load speed of the motor close to its no-load speed.
3	(c)	(i)	1	
3	(c)	(ii)	1 1	Synoptic mark from Unit 1: 1.3 Synoptic mark from Unit 1: 1.3
3	(c)	(iii)	1	Allow ecf from i and ii

Question	Answer	Marks	Guidance
<p>4 (a)</p>		<p>2</p>	<p>1 mark for each correct letter (E and D) in the correct boxes.</p>
<p>4 (b) (i)</p>	<p>Box 3: smoothing circuit (accept: smoother, capacitor or condenser)</p> <p>Box 4 stabilising circuit (accept: stabiliser, [voltage/current/load] regulator)</p>	<p>1</p> <p>1</p>	
<p>4 (b) (ii)</p>	<p>Maintains constant [or little change in] voltage [or current] (wtte)</p> <p>Regardless of the load on the output (wtte)</p>	<p>1</p> <p>1</p>	<p>Accept 'regardless of current drawn' if constant or little change in voltage</p>

Question			Answer	Marks	Guidance
4	(c)	(i)	<p>Any 3 from</p> <ul style="list-style-type: none"> • Correct symbols for LED and resistor (do not allow variable resistor or thermistor etc) – 1 mark • Resistor and LED labelled – 1 mark • Components in series with power supply – 1 mark • Correct polarity for LED (for any symbol recognizable as a diode) – 1 mark 	3	<p>The first diagram shows a circuit with a +3.3 V supply at the top and a 0 V terminal at the bottom. An LED is connected in series with a resistor. The LED is at the top, with its cathode pointing towards the 0 V terminal. The resistor is at the bottom. The LED is labeled 'LED' and the resistor is labeled 'Resistor'.</p> <p>OR</p> <p>The second diagram shows a similar circuit with a +3.3 V supply at the top and a 0 V terminal at the bottom. A resistor is connected in series with an LED. The resistor is at the top, and the LED is at the bottom, with its cathode pointing towards the 0 V terminal. The resistor is labeled 'Resistor' and the LED is labeled 'LED'.</p>
4	(c)	(ii)	<p>To stop <u>too much current flowing through the LED</u> (wtte)</p> <p>To <u>prevent the LED from overheating</u> (wtte)</p>	1 1	<p>Clear that it is LED current that is being limited</p> <p>Accept: preventing damage/blowing/melting of LED</p> <p>Alternative explanation considering the role of the current limiting resistor in prevention of damage to other components in the circuit can be awarded a maximum of 1 mark</p>

Question		Answer	Marks	Guidance												
5	(a)	One mark for each correct answer	3													
		<table border="1"> <thead> <tr> <th>input voltage</th> <th>output voltage</th> <th>voltage gain</th> </tr> </thead> <tbody> <tr> <td>3.0</td> <td>1.5</td> <td>0.5</td> </tr> <tr> <td>-2.5</td> <td>-7.5</td> <td>3</td> </tr> <tr> <td>-4</td> <td>6</td> <td>-1.5</td> </tr> </tbody> </table>			input voltage	output voltage	voltage gain	3.0	1.5	0.5	-2.5	-7.5	3	-4	6	-1.5
		input voltage			output voltage	voltage gain										
		3.0			1.5	0.5										
-2.5	-7.5	3														
-4	6	-1.5														
5	(b)	2 resistor values in correct ratio $R_F:R_2 = 1:2$	2	If resistor values incorrect award 1 mark for evidence of correct formula used: Voltage Gain = $1 + R_F/R_2$												
5	(c)	input connected to non-inverting input only (ignore any input resistor) output connected to op-amp output feedback resistor from output to inverting input only resistor from inverting input to 0V only R_F and R_2 correctly labelled	1 1 1 1	Allow V_{in} for input and V_{out} for output 												

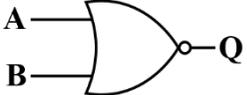Question			Answer	Marks	Guidance															
6	(a)		<p>Start of sentence</p> <p>End of sentence</p> <p>When a T-type flip-flop is triggered and T is low, ...</p> <p>When a T-type flip-flop is triggered and T is high, ...</p> <p>...Q changes.</p> <p>...Q stays the same.</p> <p>...T changes.</p> <p>...the clock is \bar{T}.</p>	2	1 mark for each correct line															
6	(b)	(i)	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Q	0	0	1	0	1	0	1	0	0	1	1	0	1	All combinations of A and B (any order)
A	B	Q																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		
6	(b)	(ii)	NOR [gate]	1																
6	(b)	(iii)		1																
6	(b)	(iv)	$Q = \overline{A + B}$	1																

Question		Answer				Marks	Guidance
6	(c)		G	H	J	K	1 1 1 1 1 mark for each correct column allow ecf from G to H allow ecf from G to J allow ecf from H and J to K
		1	0	1	0		
		1	0	0	0		
		0	1	1	1		
		0	1	1	1		
		1	0	1	0		
		1	0	0	0		
		0	0	1	0		
		0	0	1	0		

OCR (Oxford Cambridge and RSA Examinations)
The Triangle Building
Shaftesbury Road
Cambridge
CB2 8EA

OCR Customer Contact Centre

Education and Learning

Telephone: 01223 553998

Facsimile: 01223 552627

Email: general.qualifications@ocr.org.uk

www.ocr.org.uk

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored

Oxford Cambridge and RSA Examinations
is a Company Limited by Guarantee
Registered in England
Registered Office; The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA
Registered Company Number: 3484466
OCR is an exempt Charity

OCR (Oxford Cambridge and RSA Examinations)
Head office
Telephone: 01223 552552
Facsimile: 01223 552553

© OCR 2022

 **Cambridge
Assessment**

