

**CAMBRIDGE TECHNICALS LEVEL 3 (2016)**

**Examiners' report**

# **ENGINEERING**

**05822–05825, 05873**

**Unit 4 January 2022 series**

# Contents

|                                 |    |
|---------------------------------|----|
| Examiners' report template..... | i  |
| Contents.....                   | 2  |
| Introduction .....              | 3  |
| Unit 4 series overview .....    | 4  |
| Question 1 (a) (i).....         | 5  |
| Question 1 (a) (ii) .....       | 6  |
| Question 1 (b).....             | 6  |
| Question 1 (c) .....            | 7  |
| Question 1 (d).....             | 7  |
| Question 1 (e).....             | 7  |
| Question 2 (a) (i).....         | 8  |
| Question 2 (a) (ii) .....       | 9  |
| Question 2 (a) (iii) .....      | 9  |
| Question 2 (a) (iv).....        | 10 |
| Question 2 (a) (v).....         | 10 |
| Question 3 (a).....             | 11 |
| Question 3 (b).....             | 12 |
| Question 3 (c) (i).....         | 12 |
| Question 3 (c) (ii) .....       | 13 |
| Question 3 (c) (iii).....       | 13 |
| Question 4 (a).....             | 14 |
| Question 4 (b) (i).....         | 15 |
| Question 4 (b) (ii) .....       | 15 |
| Question 4 (c) (i).....         | 16 |
| Question 4 (c) (ii) .....       | 16 |
| Question 5 (a).....             | 17 |
| Question 5 (b).....             | 17 |
| Question 5 (c).....             | 18 |
| Question 6 (a).....             | 19 |
| Question 6 (b) (i).....         | 19 |
| Question 6 (b) (ii) .....       | 20 |
| Question 6 (b) (iii) .....      | 20 |
| Question 6 (b) (iv).....        | 21 |
| Question 6 (c).....             | 21 |

## Introduction

Our examiners' reports are produced to offer constructive feedback on candidates' performance in the examinations. They provide useful guidance for future candidates.

The reports will include a general commentary on candidates' performance, identify technical aspects examined in the questions and highlight good performance and where performance could be improved. The reports will also explain aspects which caused difficulty and why the difficulties arose, whether through a lack of knowledge, poor examination technique, or any other identifiable and explainable reason.

Where overall performance on a question/question part was considered good, with no particular areas to highlight, these questions have not been included in the report.

A full copy of the question paper and the mark scheme can be downloaded from OCR.

### Would you prefer a Word version?

Did you know that you can save this PDF as a Word file using Acrobat Professional?

Simply click on **File > Export to** and select **Microsoft Word**

(If you have opened this PDF in your browser you will need to save it first. Simply right click anywhere on the page and select **Save as . . .** to save the PDF. Then open the PDF in Acrobat Professional.)

If you do not have access to Acrobat Professional there are a number of **free** applications available that will also convert PDF to Word (search for PDF to Word converter).


## Unit 4 series overview

As with previous series, candidates taking the Principles of Electrical and Electronic Engineering exam seemed particularly confident with the electronic content and particularly digital. Most challenging was DC theory and the application of Ohm's Law, Kirchoff's Laws, and the resistor equivalency formula. Candidates who had revised and committed to memory circuit diagrams performed well as did those able to handle the algebra required to use the formula booklet successfully.

| <b><i>Candidates who did well on this paper generally did the following:</i></b>   | <b><i>Candidates who did less well on this paper generally did the following:</i></b>  |
|--|--|
| <ul style="list-style-type: none"> <li>• Recalled circuit symbols for electrical components.</li> <li>• Had the knowledge of algebra required to use the formula in the formula booklet to solve an equation for an unknown.</li> <li>• Could confidently apply Kirchoff's first and second laws.</li> <li>• Could confidently recall circuit diagrams for op amps and motors.</li> <li>• Wrote clearly with any changes/corrections to responses being clearly understood, e.g. when changing responses in the truth table there was no ambiguity.</li> </ul> | <ul style="list-style-type: none"> <li>• Did not carefully draw circuit diagrams, and missed some labelling where required, or symbols were drawn inaccurately.</li> <li>• Did not successfully handle prefixes to give the correct response to the correct power of ten.</li> <li>• Did not always include correct units.</li> <li>• Did not attempt or gave incorrect/weak responses to questions looking for an explanation.</li> <li>• Did not give a response to all of the numerical questions and were therefore unable to access later parts of the question (candidates should be attempting all parts, as error carried forward marking for subsequent questions is given).</li> </ul> |

### Question 1 (a) (i)

1 The circuit diagram in **Fig. 1** shows a network of resistors.

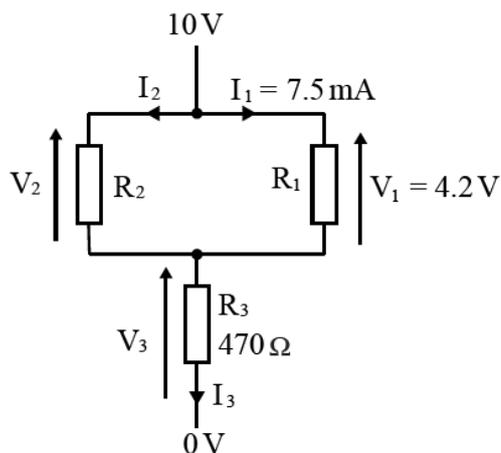

**Fig. 1**

(a) A voltmeter is used to measure the voltage  $V_1$ .

(i) Draw **on Fig. 1** to show how a voltmeter should be connected to measure the voltage  $V_1$ .

[1]

The majority of candidates answered this question successfully showing the voltmeter connected in parallel across resistor  $R_1$ . However, there were many responses where the voltmeter symbol did not appear to be familiar to the candidate with alternative symboling used, which was accepted within the context of this question but in future series may not be, so candidates should be familiar with the symbols for meters.

|  |                   |   |
|--|-------------------|---|
|  | <p><b>AfL</b></p> | <p>Candidates should be familiar with the symbols for the main electrical meters i.e. voltmeter, ammeter, and ohmmeter and how they are connected in a circuit.</p> |
|--|-------------------|---|

Question 1 (a) (ii)

(ii) A multimeter is used as a voltmeter to measure the voltage  $V_1$ .

Fig. 2a shows a multimeter with the dial in the off position.

Draw an arrow on Fig. 2b showing the correct position of the dial to precisely measure the voltage  $V_1$ .

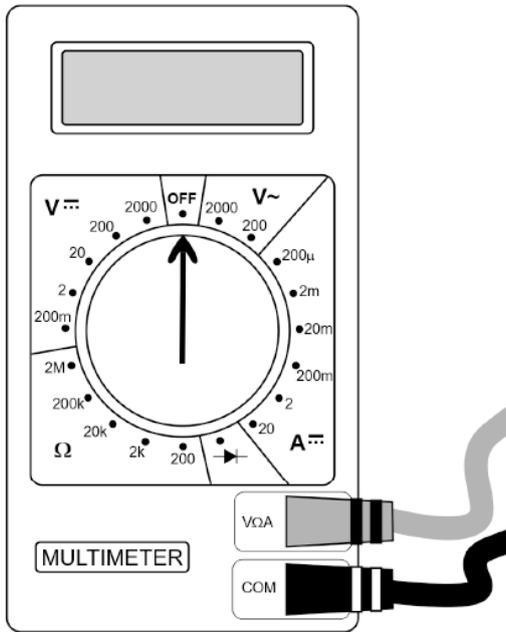


Fig. 2a

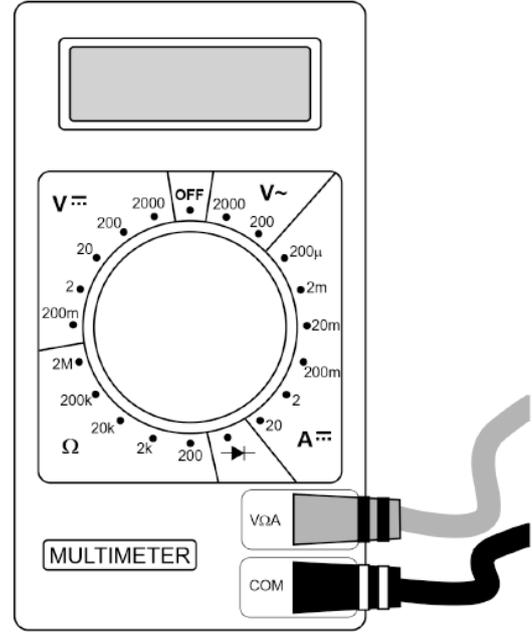


Fig. 2b

[1]

Although the majority of candidates responded correctly with the 20V DC setting, a significant minority opted for either the 2V or attempted to choose a value between the 2V and 20V, with very few choosing an alternative response.

Question 1 (b)

(b) Calculate the value of the resistor  $R_1$ .

$R_1 = \dots\dots\dots \Omega$  [1]

This question was handled well with the majority of candidates comfortable using Ohm's Law. The most common error was ignoring the milli prefix on the current.

### Question 1 (c)

(c) Calculate the voltage  $V_3$ .

$$V_3 = \dots\dots\dots \text{ V [1]}$$

This question was much less successfully handled with candidates struggling to apply Kirchoff's second law. Frequently seen incorrect responses were 10V and 4.2V. Candidates should be familiar with the use of this law in a range of contexts both with full circuit diagrams and resistor networks, as in this question.

### Question 1 (d)

(d) Calculate the current  $I_3$ .

$$I_3 = \dots\dots\dots \text{ A [1]}$$


Again candidates coped well with this application of Ohm's Law, with the vast majority being able to divide their response to 1c by 470 ohms.

### Question 1 (e)

(e) Calculate the value of the resistor  $R_2$ .

$$R_2 = \dots\dots\dots \Omega [2]$$

This question was only answered successfully by the most able candidates. The majority were unable to access the first mark which required use of Kirchoff's second law to determine voltage and Kirchoff's first law to determine current, with a significant minority incorrectly adding  $I_3$  to  $I_1$  to get  $I_2$ .
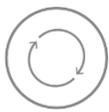
|   |                   |  |
|---|-------------------|--|
|  | <p><b>AfL</b></p> | <p>Candidates should be given opportunity to apply Kirchoff's first and second laws to a range of simple circuits and resistor networks.</p> |
|---|-------------------|--|

## Question 1 (f)

- (f) Calculate the resistance of the network of resistors.

resistance of the network of resistors = .....  $\Omega$  [2]

Candidates that were able to identify that  $R_1$  and  $R_2$  were connected in parallel in general applied the parallel formula successfully. The majority of candidates were able to access the second mark for adding 470 Ohms (for a resistor in series) onto their calculated value of  $R_1$  and  $R_2$ .

## Question 2 (a) (i)

- 2 (a) A sine wave alternating current (AC) supply of frequency  $f = 455$  kHz is connected in series with a resistor ( $R$ ), a capacitor ( $C$ ) and an inductor ( $L$ ).

- (i) Draw a diagram of the circuit.

Label all components.

[2]

Although the majority of candidates appeared familiar with the symbols for a resistor, capacitor, inductor, and AC supply, a significant minority were unable to draw all accurately and many did not follow the instructions to label all components. On a significant minority of papers, one of the symbols was omitted entirely.


Question 2 (a) (ii)

(ii) The value of inductor  $L = 240 \mu\text{H}$ .

Calculate the reactance  $X_L$  of the inductor when the frequency  $f = 455 \text{ kHz}$ .

$X_L = \dots\dots\dots \Omega$  [3]

The vast majority of candidates were able to select and use the correct formula with marks predominantly being lost due to incorrect handling of prefixes.
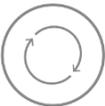
|  |            |   |
|--|------------|---|
|  | <b>AfL</b> | Candidates should be familiar with the use of prefixes. |
|--|------------|---|

Question 2 (a) (iii)


(iii) The reactance of the capacitor  $X_C = 910 \Omega$  when the frequency  $f = 455 \text{ kHz}$ .

Calculate the value of the capacitor ( $C$ ).

Give the units for your answer.

$C = \dots\dots\dots$  [3]

Candidates seemed far less familiar with using this equation to find  $C$  rather than  $X_C$  with many failing to substitute correctly. Of those that did substitute correctly only a minority were able to successfully rearrange the equation. The units of capacitance were not well known as Farad (F) with many candidates selecting Henry, Ohm or just using  $C$ .
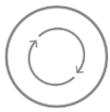
|   |                   |   |
|---|-------------------|---|
|  | <p><b>AfL</b></p> | <p>Candidates should have the level of algebra required to use all equations in the formula booklet, rearranging as appropriate.</p> <p>Standard units for all variables should be learned.</p> |
|---|-------------------|---|

**Question 2 (a) (iv)**

(iv) The value of the resistor  $R = 330 \Omega$ .

Calculate the impedance ( $Z$ ) of the circuit at a frequency of 455 kHz.

$Z = \dots\dots\dots \Omega$  [2]

Although many candidates were able to select the correct formula from the formula booklet (with the most common error being using the RL or RC formula instead of RLC) a significant number of candidates substituted the value for C into the equation rather than  $X_C$ .

**Question 2 (a) (v)**

(v) Calculate the amplitude of the current in the circuit when it is supplied with a sine wave of amplitude 15 V at a frequency of 455 kHz.

Use the equation  $I = \frac{V}{Z}$


$I = \dots\dots\dots A$  [1]

This question was handled well with almost all candidates able to divide 15 by their answer to Question 2 (a) (iv) to secure the mark. The majority of incorrect responses were from candidates who did not attempt the question.

### Question 3 (a)

3 An electric food mixer uses a shunt-wound DC motor.

- (a) Draw **on Fig. 3** to show how a field winding and armature should be connected to a 14.4 V power supply in a shunt-wound DC motor.

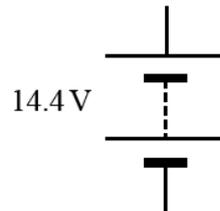

**Fig. 3**

[2]

The symbol for field winding appeared far more familiar than that for an armature with many candidates appearing to need practice with drawing this. However, the question was well handled in general with a small minority drawing the symbols in series rather than parallel.

### Question 3 (b)

- (b) Complete the sentences in the paragraph below by choosing the most appropriate words from the list.

Use each word once, more than once or not at all.

- constant**
- increased**
- infinite**
- reduced**
- zero**

A shunt-wound DC motor maintains a fairly constant speed regardless of load.

When the motor is running with no load, it spins at high speed.

When a load is applied to the motor, the speed reduces, and the EMF generated in the armature is .....

This means that the current in the armature is increased and so the torque is .....

The current in the field winding is .....

All of this keeps the load speed of the motor close to its no-load speed.

[3]

This question was not well handled with only a minority of candidates able to show an understanding of electrical theory in a shunt wound motor.

### Question 3 (c) (i)

- (c) The shunt-wound motor has a field winding resistance ( $R_f$ ) of  $48 \Omega$  and an armature winding resistance ( $R_a$ ) of  $18 \Omega$ .

- (i) Calculate the current in the field winding ( $I_f$ ) when 14.4 V is supplied to the motor.

$I_f = \dots\dots\dots$  A [1]

The application of Ohm's Law was attempted by most but some candidates attempted to include the armature resistance in their calculation.

**Question 3 (c) (ii)**

- (ii) The motor operates from a 14.4 V power supply ( $V$ ).

When the motor is turning at high speed, it produces a back EMF ( $E$ ) of 12.2 V.

Calculate the armature current ( $I_a$ ) in the motor.

Use the equation  $V = E + I_a R_a$

$$I_a = \dots\dots\dots \text{ A [2]}$$

Although the correct equation was given, a minority were able to handle the algebra required to rearrange the equation successfully to come to the correct answer.

**Question 3 (c) (iii)**

- (iii) Calculate the total current ( $I_t$ ) drawn from the power supply when the motor is turning at high speed.

$$I_t = \dots\dots\dots \text{ A [1]}$$

The majority of candidates were able to apply the correct formula and add their Question 3 (c)(i) to their Question 3 (c)(ii) to find the total current.

Question 4 (a)

4 (a) The block diagram and circuit diagram for a power supply are shown in Fig. 4.

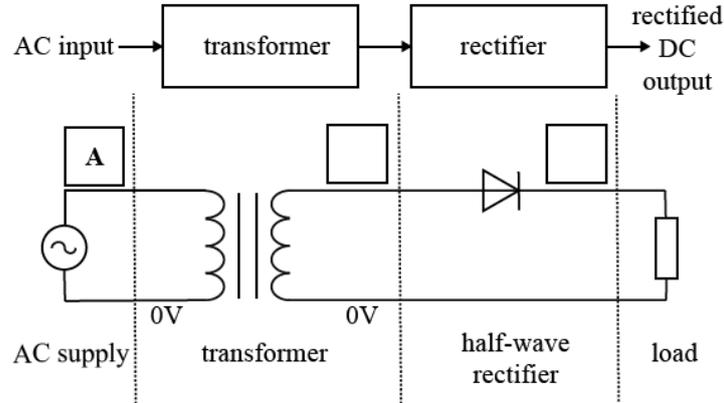


Fig. 4

Graphs A-E in Fig. 5 show how voltage can change over time.

In Fig. 4, the letter A indicates that Graph A shows the way that voltage changes over time at this point in the circuit.

Fill in the two blank boxes  in Fig. 4 to show which graph (B, C, D or E) represents the way that voltage changes over time at each point in the circuit.

[2]

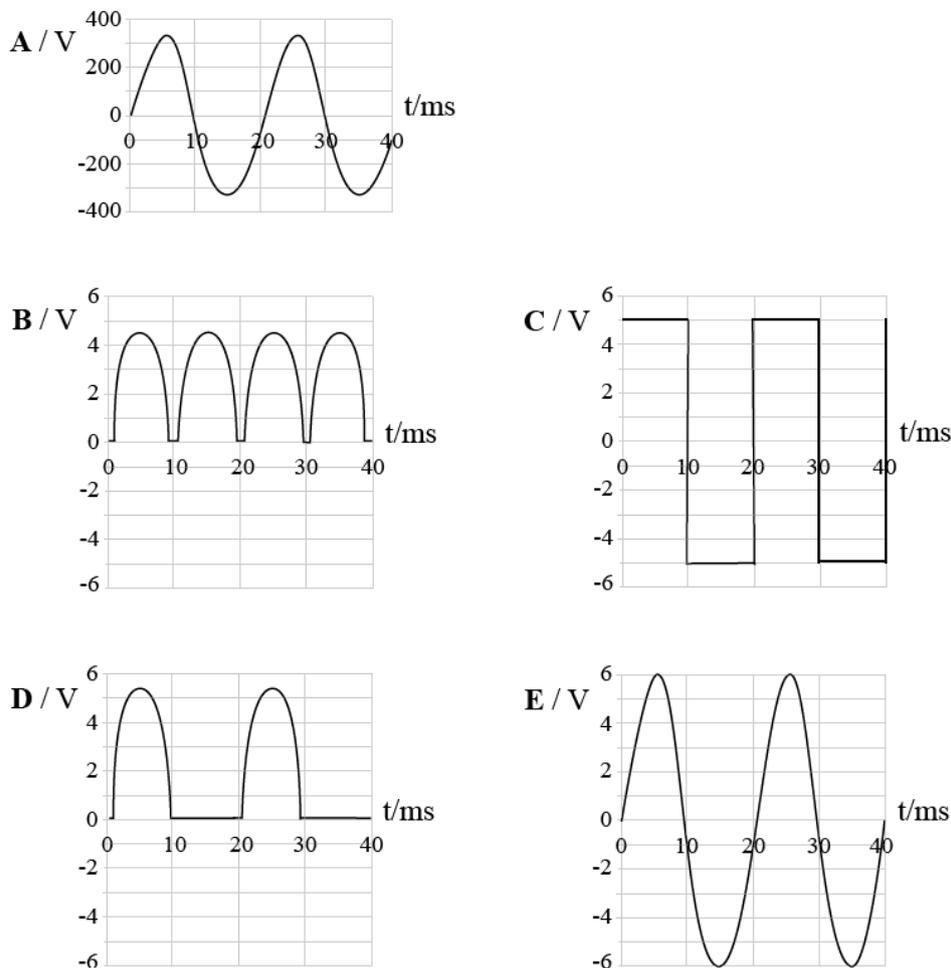


Fig. 5

Most candidates were able to score at least 1 mark for this question with the trace after the transformer being attempted the most successfully. Many candidates chose the full rectification pattern although a single diode would give half wave rectification.

### Question 4 (b) (i)

(b) An incomplete block diagram of a stabilised power supply is shown in Fig. 6.

(i) Add the names of the **two** missing blocks to complete the stabilised power supply.

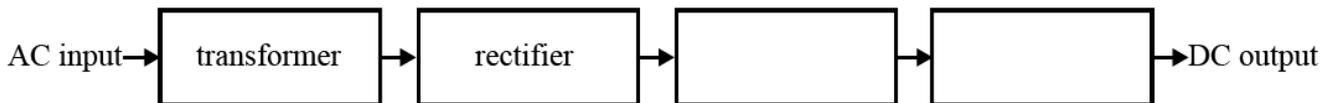


Fig. 6

[2]

The majority of candidates responded with smoothing and stabilising although a significant minority listed them in the wrong order. The question was occasionally left blank and the most common alternative was to give 'capacitor' for 'smoothing'.

### Question 4 (b) (ii)

(ii) A stabilised power supply has good load regulation.

Explain what is meant by good load regulation.

.....

.....

.....

..... [2]

This question should be familiar to candidates with the response being straight from the specification. However, many candidates appeared unfamiliar with load regulation mentioning that the load value (rather than the voltage or current) remained constant or did not change much. Candidates who started with the fact that the voltage or current remained constant often went on to give confused explanations attempting to relate energy or power. A minority of candidates were able to identify that the voltage or current remained the same with varying load.

### Question 4 (c) (i)

(c) An LED is used to show that the DC output of a 3.3 V power supply is operating.

(i) Complete **Fig. 7** to show how an LED and current limiting resistor can be used to show that the power is operating.

Label the parts in your diagram.

+3.3 V —————

0 V —————

**Fig. 7**

[3]

Although the majority of candidates drew two symbols in series, the LED symbol was not well known, often being drawn as a lamp or a combination of a triangle and arrow shape, and many candidates incorrectly assumed the current limiting resistor to be a variable resistor.

### Question 4 (c) (ii)

(ii) Explain the function of the current limiting resistor in **Fig. 7**.

.....

.....

.....

..... [2]

Many candidates incorrectly stated that the purpose of a current limiting resistor was either to allow the LED to be dimmed or to act as a fuse, melting when current was too high.

|   |                             |   |
|---|-----------------------------|---|
|  | <p><b>Misconception</b></p> | <p>Candidates should be confident of the role of a current limiting resistor in protection of other components (particularly LEDs) from the heating effect of high current as opposed to a general protection of the 'circuit'.</p> |
|---|-----------------------------|---|

### Question 5 (a)

- 5 (a) The table shows the input voltage ( $V_{in}$ ), output voltage ( $V_{out}$ ) and voltage gain of three different amplifiers.

Complete the table with the missing values.

Use the equation: Voltage Gain =  $\frac{V_{out}}{V_{in}}$

| Input voltage ( $V_{in}$ ) | Output voltage ( $V_{out}$ ) | Voltage gain |
|----------------------------|------------------------------|--------------|
| 3.0                        | 1.5                          |              |
| -2.5                       |                              | 3            |
|                            | 6                            | -1.5         |

[3]

The majority of candidates were given marks for this question with the voltage gain being the most successful calculation. The rearrangement to find  $V_{in}$  was the most challenging, with many candidates giving the reciprocal due to difficulty with the algebra involved. The handling of the negative numbers could be improved, with some candidates giving all answers as positive numbers.

### Question 5 (b)

- (b) Calculate the resistors for a non-inverting operational amplifier, constructed from an operational amplifier (op-amp) with a voltage gain of 1.5.

Use the equation: Voltage Gain =  $1 + \frac{R_F}{R_2}$

$R_F = \dots\dots\dots \text{ k}\Omega$

$R_2 = \dots\dots\dots \text{ k}\Omega$


[2]

The vast majority of candidates were given marks for this question being able to use the formula given to realise that the ratio of resistors was required to be 1:2.

**Question 5 (c)**

(c) Complete **Fig. 8** to show a non-inverting amplifier.

Label the input, output,  $R_F$  and  $R_2$ .

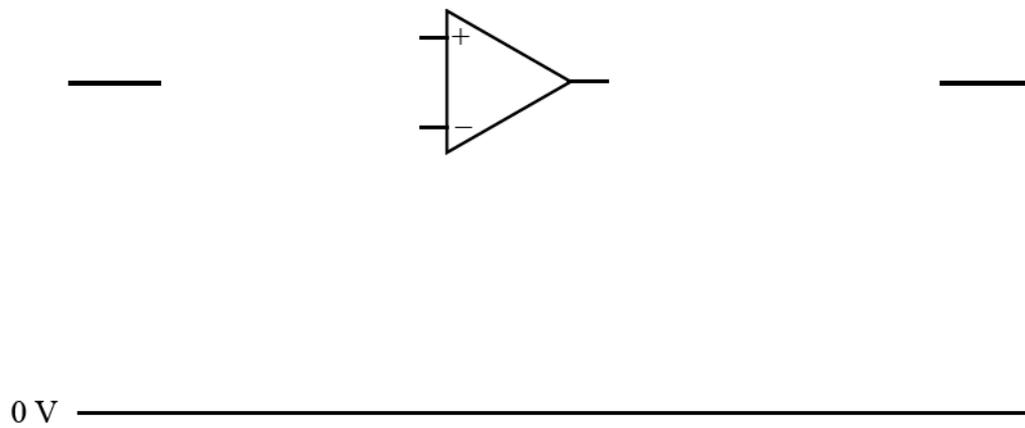

**Fig. 8**

[5]

This question led to a mixed response from candidates, some of whom were fully prepared to recall the diagram and others who made little or no attempt. Many candidates had not read the question carefully and so neglected to label the input, output,  $R_F$  and  $R_2$  as required. The most common error was to draw the feedback loop giving positive feedback.

### Question 6 (a)

6 (a) The circuit symbol for a T-type flip-flop is shown in Fig. 9.

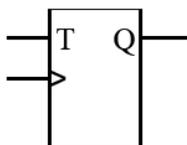


Fig. 9

Draw a line to join the start of each sentence to the most appropriate end of sentence about the behaviour of a T-type flip-flop.

There will be some end of sentences without a connecting line.

**Start of sentence**

**End of sentence**

When a T-type flip-flop is triggered and T is low, ...

...Q changes.

...Q stays the same.

When a T-type flip-flop is triggered and T is high, ...

...T changes.

...the clock is  $\bar{T}$ .

[2]

The majority of candidates gained at least 1 mark however, incorrect responses were wide-ranging from the alternatives given.

### Question 6 (b) (i)

(b) A partially complete truth table for a logic gate is shown below.

| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
|   |   | 0 |
|   |   | 0 |
|   |   | 0 |

(i) Complete the truth table by filling in columns A and B.

[1]


As the three remaining options did not have to be given in any particular order, the vast majority of candidates answered this question successfully.

**Question 6 (b) (ii)**

**(ii)** Name the logic gate described by the truth table.

..... [1]

Candidates appeared to find difficulty with identifying the name of the logic gate from the truth table.
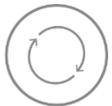
|   |                   |  |
|---|-------------------|--|
|  | <p><b>AfL</b></p> | <p>When given either a logic gate name, circuit symbol, truth table or Boolean expression, candidates should be able to provide the rest of the information listed. It was apparent that candidates were not as used to identifying a gate from its truth table as they were recalling a truth table when given the logic circuit symbol/name.</p> |
|---|-------------------|--|

**Question 6 (b) (iii)**

**(iii)** Draw the circuit symbol for the logic gate described by the truth table.

Label the inputs **A** and **B** and label the output **Q**.

[1]

The majority of candidates that had answered Question 6 (b) (ii) correctly were able to gain this mark. Common errors were to draw the incorrect gate named in Question 6 (b) (ii), although the question did refer the candidate back to the truth table, or to omit the labelling of the inputs A and B and the output Q on the circuit symbol.

### Question 6 (b) (iv)

(iv) Put a **ring** around the correct Boolean expression for the logic gate described by the truth table.

$Q = A + B$       $Q = \overline{A + B}$       $Q = A \cdot B$       $Q = \overline{A \cdot B}$       $Q = A \oplus B$

[1]

Candidates seemed familiar with the Boolean expressions and a small majority were able to match the correct expression to the truth table.

### Question 6 (c)

(c) Fig. 10 shows a logic gate circuit.

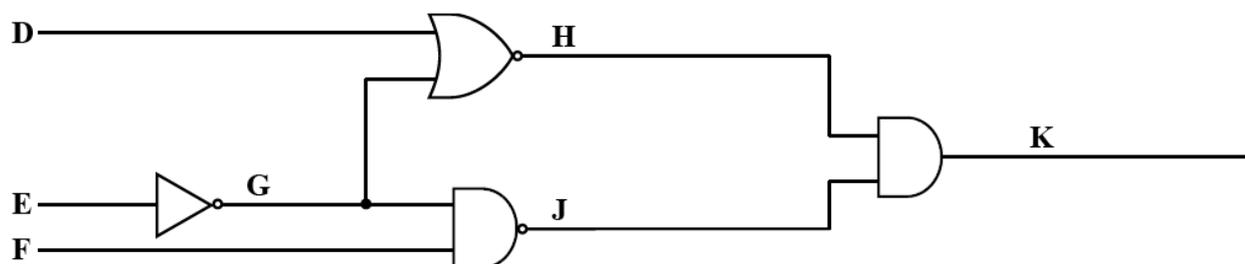


Fig. 10

Complete the truth table for this circuit.

| D | E | F | G | H | J | K |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 |   |   |   |   |
| 0 | 0 | 1 |   |   |   |   |
| 0 | 1 | 0 |   |   |   |   |
| 0 | 1 | 1 |   |   |   |   |
| 1 | 0 | 0 |   |   |   |   |
| 1 | 0 | 1 |   |   |   |   |
| 1 | 1 | 0 |   |   |   |   |
| 1 | 1 | 1 |   |   |   |   |

[4]

The vast majority of candidates were confident completing the truth table for the NOT gate with slightly fewer being comfortable with the AND gate. However the NOR and NAND gates seemed to pose more of a challenge with many candidates obtaining incorrect responses for columns H and J.

## Copyright information

Any reference to existing companies or organisations is entirely coincidental and is not intended as a depiction of those companies or organisations.

---

# Supporting you

---

## Review of results

If any of your students' results are not as expected, you may wish to consider one of our review of results services. For full information about the options available visit the [OCR website](#).

## Supporting you through 2021-2022

Our priority is supporting you and your students this spring and to support you as you prepare for summer 2022. We'll update our [website information](#) regularly with resources, guidance and key information.

## Take a look at our support for:

- [Teachers](#)
- [Students](#)
- [Exams officers](#)

## Keep up-to-date

We are sending a weekly roundup to tell you about important updates. You can also sign up for your subject specific updates. If you haven't already, [sign up here](#).

## OCR Professional Development

Attend one of our popular CPD courses to hear directly from a senior assessor or drop in to a Q&A session. All our courses for the academic year 2021-2022 are being delivered live via an online platform, so you can attend from any location.

Please find details for all our courses on the relevant subject page on our [website](#) or visit [OCR professional development](#).

## Signed up for Exambuilder?

**ExamBuilder** is the question builder platform for a range of our GCSE, A Level, Cambridge Nationals, Cambridge Technicals and Functional Skills qualifications. See the full list of available qualifications in the [sign up form](#).

ExamBuilder is **free for all OCR centres** with an Interchange account and gives you unlimited users per centre. We need an [Interchange](#) username to validate the identity of your centre's first user account for ExamBuilder.

If you do not have an Interchange account please contact your centre administrator (usually the Exams Officer) to request a username, or nominate an existing Interchange user in your department.

---

# Supporting you

---

## Active Results

Review students' exam performance with our free online results analysis tool.

**For the spring 2022 series, results analysis is available for Cambridge Nationals (moderated units) only.**

It allows you to:

- review and run analysis reports on exam performance
- analyse results at question and/or topic level
- compare your centre with OCR national averages
- identify trends across the centre
- facilitate effective planning and delivery of courses
- identify areas of the curriculum where students excel or struggle
- help pinpoint strengths and weaknesses of students and teaching departments.

Find out more at [ocr.org.uk/activeresults](https://ocr.org.uk/activeresults).

## Need to get in touch?

If you ever have any questions about OCR qualifications or services (including administration, logistics and teaching) please feel free to get in touch with our customer support centre.

Call us on  
**01223 553998**

Alternatively, you can email us on  
**support@ocr.org.uk**

For more information visit

 **ocr.org.uk/qualifications/resource-finder**

 **ocr.org.uk**

 **/ocrexams**

 **/ocrexams**

 **/company/ocr**

 **/ocrexams**

## We really value your feedback

Click to send us an autogenerated email about this resource. Add comments if you want to. Let us know how we can improve this resource or what else you need. Your email address will not be used or shared for any marketing purposes.



**I like this**



**I dislike this**

Please note – web links are correct at date of publication but other websites may change over time. If you have any problems with a link you may want to navigate to that organisation's website for a direct search.



OCR is part of Cambridge University Press & Assessment, a department of the University of Cambridge.

For staff training purposes and as part of our quality assurance programme your call may be recorded or monitored. © OCR 2022 Oxford Cambridge and RSA Examinations is a Company Limited by Guarantee. Registered in England. Registered office The Triangle Building, Shaftesbury Road, Cambridge, CB2 8EA. Registered company number 3484466. OCR is an exempt charity.

OCR operates academic and vocational qualifications regulated by Ofqual, Qualifications Wales and CCEA as listed in their qualifications registers including A Levels, GCSEs, Cambridge Technicals and Cambridge Nationals.

OCR provides resources to help you deliver our qualifications. These resources do not represent any particular teaching method we expect you to use. We update our resources regularly and aim to make sure content is accurate but please check the OCR website so that you have the most up to date version. OCR cannot be held responsible for any errors or omissions in these resources.

Though we make every effort to check our resources, there may be contradictions between published support and the specification, so it is important that you always use information in the latest specification. We indicate any specification changes within the document itself, change the version number and provide a summary of the changes. If you do notice a discrepancy between the specification and a resource, please [contact us](#).

You can copy and distribute this resource freely if you keep the OCR logo and this small print intact and you acknowledge OCR as the originator of the resource.

OCR acknowledges the use of the following content: N/A

Whether you already offer OCR qualifications, are new to OCR or are thinking about switching, you can request more information using our [Expression of Interest form](#).

Please [get in touch](#) if you want to discuss the accessibility of resources we offer to support you in delivering our qualifications.